
Olteanu Iulia,314CC

Circuit R-L serie

Circuit R-C serie

Olteanu Iulia,314CC


Circuit R-L-C serie

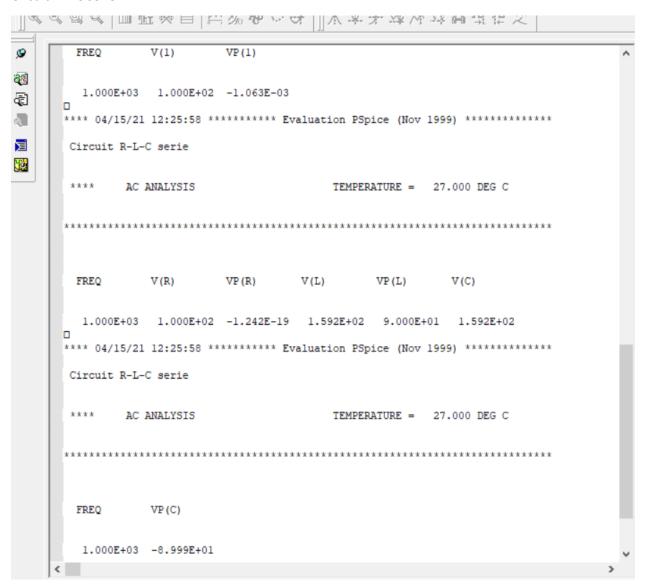



Olteanu Iulia,314CC


Transfer maxim de putere

Rezonanta serie

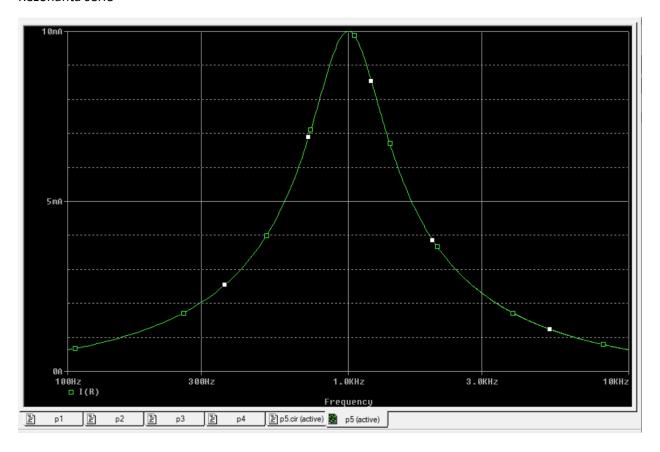


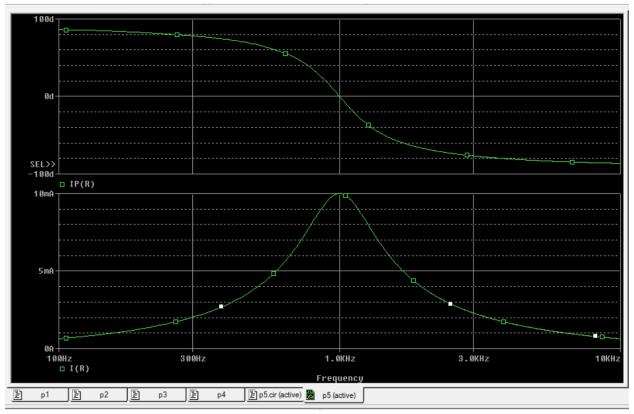


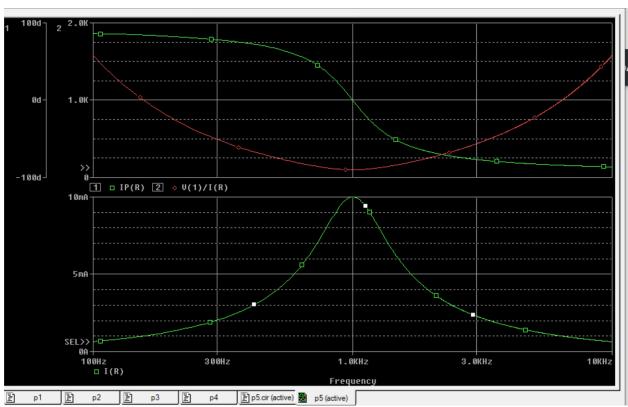

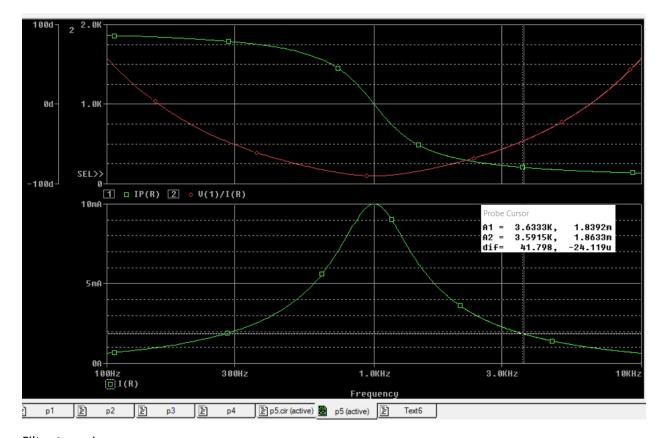


Filtru trece-jos

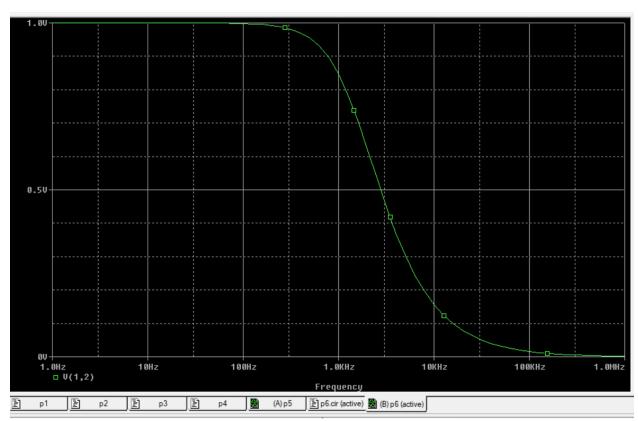


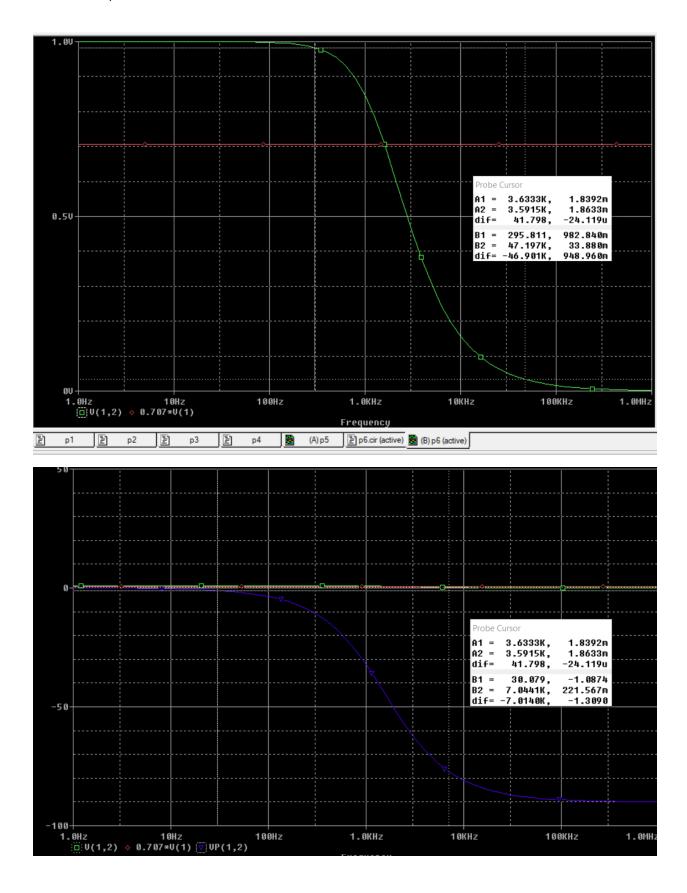


Filtru trece-banda de tip Butterworth

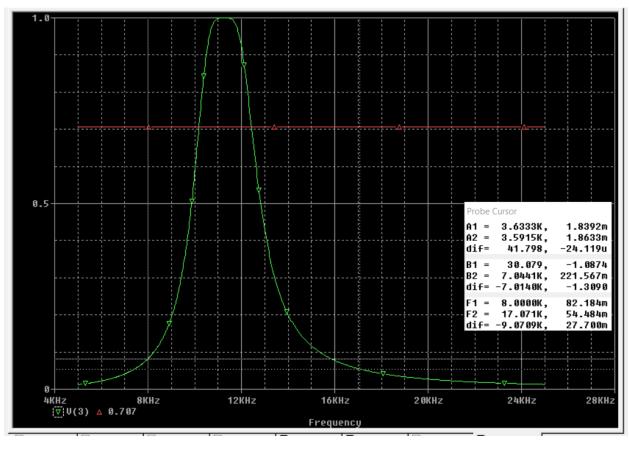


Filtrul opreste-banda

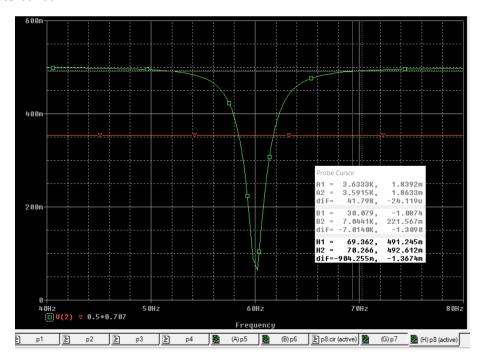

Problema 1.1

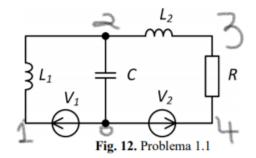

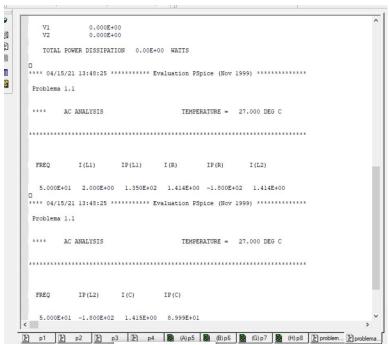

```
Problema 1.1
V1 1 0 AC 20 -45
L1 1 2 31.84M
L2 2 3 95.54M
R 3 4 10
V2 4 0 AC 60 45
C 2 0 159.15u
.AC LIN 1 50 50
.PRINT AC I(L1) IP(L1) I(R) IP(R) I(L2) IP(L2) I(C) IP(C)
.END
```

Problema 1.2



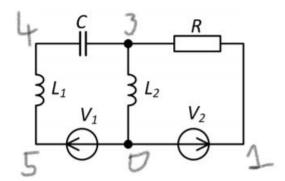


Fig. 13. Problema 1.2

```
Problema 1.2
V1 5 0 AC 28.28 -90
V2 1 0 AC 20 135
L1 5 4 63.7m
L2 3 0 31.85m
C 4 3 318.47u
R 3 1 10
.AC LIN 1 50 50
.PRINT AC I(L1) IP(L1) I(R) IP(R) I(L2) IP(L2) I(C) IP(C)
.END
```

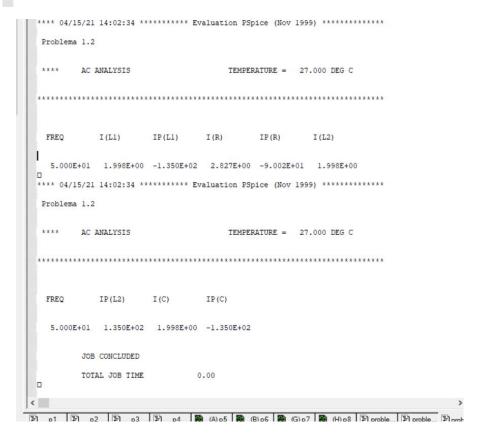

Problema 1.3

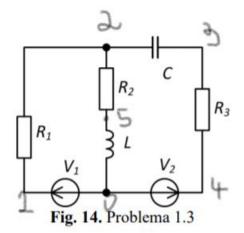

```
Problema 1.3
V1 1 0 AC 40 45
V2 4 0 AC 80 45
R1 1 2 20
R2 2 5 10
L 5 0 31.841m
C 2 3 79.61u
R3 3 4 20
.AC LIN 1 50 50
.PRINT AC I(L) IP(L) I(R1) IP(R1) I(R2) IP(R2) I(R3) IP(R3) I(C) IP(C)
.END
```